

--	--	--	--	--	--	--	--	--	--

# MULTIMEDIA UNIVERSITY

## FINAL EXAMINATION

TRIMESTER 1, 2018/2019

**EEE3096 – COMMUNICATION ELECTRONICS  
(TE)**

23th OCTOBER 2018  
9:00 A.M. – 11:00 A.M.  
(2 Hours)

---

### INSTRUCTIONS TO STUDENTS

1. This Question paper consists of 6 pages with 4 Questions only.
2. Attempt **ALL FOUR** questions.
3. Please print all your answers in the Answer Booklet provided.

Question 1

- (a) A typical system employing attenuator has four parameters that are of interest. List out these four parameters. [4 marks]
- (b) With the aids of circuit diagram, list out three types of attenuators. [6 marks]
- (c) Determine the 3 dB bandwidth of the two circuits shown in Fig. Q1c, both before and after adding a  $2\ \mu\text{H}$  inductor in series. Sketch and compare the impedance frequency response results for both circuits. Comment on the differences in terms of the bandwidth and the selectivity.

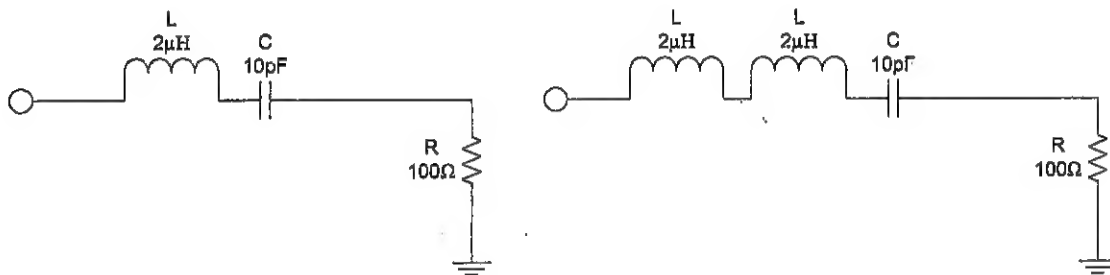


Fig. Q1c

[7 marks]

- (d) Design an impedance matching using L-network for a circuit with the source impedance  $R_S = 200\ \Omega$  and the load impedance,  $R_L = 400\ \Omega$ ,  $X_L = 0$  at a frequency of 100 MHz. Sketch and label all the values for each component of the network.

[8 marks]

Question 2

- (a) Draw the frequency response for the tuned and untuned amplifier. [3 marks]
- (b) With the aids of suitable diagrams, explain two methods of neutralization. [4 + 4 marks]

Continued .....

- (c) The transistor in Figure Q2c has the following parameters:  $r_{bb'} = 50 \Omega$ ,  $h_{fe} = 200$ ,  $V_A = 50 \text{ V}$ ,  $C_c = 12 \text{ pF}$ ,  $f_T = 250 \text{ MHz}$  and  $V_{BE} = 0.7 \text{ V}$ . The amplifier is designed to operate at  $10 \text{ MHz}$  with an operating bandwidth of  $1 \text{ MHz}$ . The transistor is biased at  $I_C = 5 \text{ mA}$ ,  $V_{CE} = 0.8 V_{CC}$  and  $I_{RBI} = 0.1 I_C$ .

- (i) Determine  $g_m$ ,  $r_{b'e}$ ,  $r_{ce}$ ,  $C_e$ ,  $R_o$  and  $C_T$

[8 marks]

- (ii) Determine the value of the inductance  $L$  and the capacitance  $C$  of the tank network.

[6 marks]

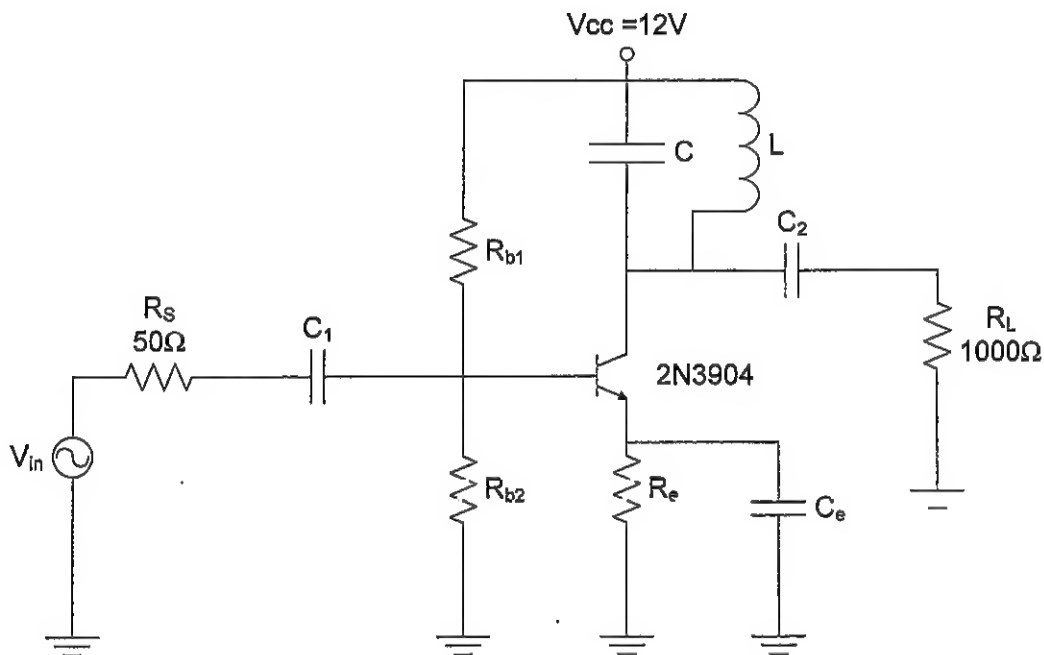


Fig. Q2c

Continued .....

Question 3

- (a) Sketch the block diagram of a Phase lock loop (PLL) and briefly explain the functions for each components of the PLL.

[4 + 8 marks]

- (b) A PLL with a voltage controlled oscillator (VCO) free-running frequency of 5 MHz has a 15 % capture range and a 30 % lock range. Over what frequency will the PLL able to capture and subsequently maintain lock?

[4 marks]

- (c) Design a PLL frequency synthesizer that will cover a frequency range of 144 to 148 MHz in 5-kHz steps, starting at 144 MHz. Assume that the reference oscillator frequency is 5 MHz, the frequency divider is fixed at  $M$  value, and the programmable frequency divider has  $N$  value, so that the synthesizer will cover the desired range.

- (i) Sketch a diagram of your PLL frequency synthesizer design, showing the frequencies present at various points of the diagram.

[4 marks]

- (ii) Determine the value  $N$  of the programmable frequency divider.

[5 marks]

Question 4

- (a) Sketch the block diagram of a black and white television (TV) receiver.

[9 marks]

- (b) Explain the basic working principle of gated automatic gain control (AGC). Explain why gated AGC is preferred over AGC using averaging or peak detector in television (TV) receivers.

[6 marks]

- (c) Give the pros and cons for Amplitude Modulation (AM) in transmitting a TV signal.

[6 marks]

- (d) Given that National Television System Committee (NTSC) defines a frame rate of 30 fps with 525 lines per frame. Determine the field and line frequency.

[4 marks]

**Continued .....**

## Appendix – Useful Formulas

### 1. L impedance matching network (when $R_L > R_S$ ):

$$B = \frac{X_L \pm \sqrt{R_L/R_S \sqrt{R_L^2 + X_L^2} - R_S R_L}}{R_L^2 + X_L^2} \quad X = \frac{1}{B} + \frac{X_L R_S}{R_L} - \frac{R_S}{B R_L}$$

$$Q = \frac{|X|}{R_S}$$

### 2. L impedance matching network (when $R_L < R_S$ ):

$$B = \pm \frac{\sqrt{(R_S - R_L)/R_L}}{R_S} \quad X = \pm \sqrt{R_L(R_S - R_L)} - X_L \quad Q = R_S |B|$$

### 3. $\pi$ impedance matching network:

$$L = L_1 + L_2 = \frac{R_L}{\omega_o} \left( \sqrt{R_S/R_L - 1} + \sqrt{R_L/R_I - 1} \right)$$

$$C_1 = \frac{1}{\omega_o R_S} \sqrt{\frac{R_S}{R_I} - 1} \quad C_2 = \frac{1}{\omega_o R_L} \sqrt{\frac{R_L}{R_I} - 1} \quad Q = \sqrt{\frac{R_S}{R_I} - 1} + \sqrt{\frac{R_L}{R_I} - 1}$$

### 4. RF Class A transistor amplifier (Hybrid $\pi$ model of BJT)

$r_{bb'}$	The base-spreading resistance.
$g_m$	The transconductance. $g_m = \frac{dI_C}{dV_{BE}} = \frac{qI_C}{kT} \cong \frac{I_C (\text{in mA})}{25.875 \text{ mV}}$ at $T=300\text{K}$ , $q$ = electronic charge, $1.6 \times 10^{-19} \text{C}$
$C_e$	The emitter capacitance.
$r_{b'e}$	The input resistance. $r_{b'e} = \frac{dV_{B'E}}{dI_B} = \frac{h_{fe}}{g_m}$
$r_{b'c}$	The collector to base resistance. $r_{b'c} = h_{fe} r_{ce}$
$C_C$	The collector capacitance.
$r_{ce}$	The output resistance. $r_{ce} \cong \frac{V_A}{I_C} = \frac{qV_A}{kTg_m}$ Where $V_A$ is known as the Early voltage and $I_C$ is the dc collector current.

Continued .....

**5. High frequency Class A amplifier parameters:****(a) Voltage gain:**

$$A_V = \frac{v_o}{v_{BE}} = -g_m R_o \frac{r_{b'e}}{r_{bb'} + r_{b'e}} \frac{1}{1 + j\omega C_T \frac{r_{bb'} r_{b'e}}{r_{bb'} + r_{b'e}}}$$

In cases where  $r_{bb'} \ll r_{b'e}$  then

$$A_V = \frac{v_o}{v_{BE}} = -\frac{g_m R_o}{1 + j\omega C_T r_{bb'}}$$

**(b) Effective voltage gain (including the effect of source impedance  $R_S$ ):**

$$A_{VS} = \frac{v_o}{V_S} = -g_m R_o \frac{r_{b'e}}{r_{bb'} + R_S + r_{b'e}} \frac{1}{1 + j\omega C_T \frac{(R_S + r_{bb'}) r_{b'e}}{R_S + r_{bb'} + r_{b'e}}}$$

In cases where  $(R_S + r_{bb'}) \ll r_{b'e}$  then

$$A_{VS} = \frac{v_o}{V_S} = -\frac{g_m R_o}{1 + j\omega C_T (R_S + r_{bb'})}$$

Where  $C_T = C_e + C_M$  and  $C_M$  = Miller capacitance  $C_M = (1 + g_m R_o) C_C$

**(c) Transition frequency**

$$f_T = \frac{1}{2\pi} \frac{g_m}{C_e + C_C}$$

**(d) Input impedance**

$$Z_I = r_{bb'} + \frac{r_{b'e}}{1 + j\omega r_{b'e} C_T}$$

End of Page

